



National Institute of Technology Patna

Department of Electronics and Communication Engineering Digital Design (EC-14102) Practice Sheet- 4

B.Tech.: Semester-I CSE- I/II

Unit: II

Date: 22/10/2024

Session: Jul-Dec 2024

Topic: Combinational Circuits

Faculty: Dr. Rajan Agrahari

Objective Questions


1. A half-adder is characterized by
 - (a) two inputs and two outputs
 - (b) three inputs and two outputs
 - (c) two inputs and three outputs
 - (d) two inputs and one output
2. A full-adder is characterized by
 - (a) two inputs and two outputs
 - (b) three inputs and two outputs
 - (c) two inputs and three outputs
 - (d) two inputs and one output
3. The inputs to a full adder are $A = 1$, $B = 0$, $C_{in} = 1$. The outputs are
 - (a) $\sum = 0$, $C_{out} = 1$
 - (b) $\sum = 1$, $C_{out} = 0$
 - (c) $\sum = 0$, $C_{out} = 0$
 - (d) $\sum = 1$, $C_{out} = 1$
4. A 3-bit parallel adder can add
 - (a) three 2-bit binary numbers
 - (b) two 3-bit binary numbers
 - (c) three bits at a time
 - (d) three bits in sequence
5. To expand a 2-bit parallel adder to a 4-bit parallel adder, you must
 - (a) use two 2-bit adders with no interconnections
 - (b) use two 2-bit adders and connect the sum outputs of one to the bit inputs of the other
 - (c) use four 2-bit adders with no interconnections
 - (d) use two 2-bit adders with the carry output of one connected to the carry input of the other
6. If a 74HC85 magnitude comparator has $A = 1000$ and $B = 1010$, the outputs are
 - (a) $A > B = 0$, $A < B = 0$, $A = B = 0$
 - (b) $A > B = 0$, $A < B = 0$, $A = B = 1$
 - (c) $A > B = 0$, $A < B = 1$, $A = B = 0$
 - (d) $A > B = 0$, $A < B = 1$, $A = B = 1$
7. If a 1-of-16 decoder with active-LOW outputs exhibits a LOW on the decimal 12 output, what are the inputs?
 - (a) $A_3A_2A_1A_0 = 1010$
 - (b) $A_3A_2A_1A_0 = 1110$
 - (c) $A_3A_2A_1A_0 = 1100$
 - (d) $A_3A_2A_1A_0 = 0100$
8. A BCD-to-7 segment decoder has 0100 on its inputs. The active outputs are
 - (a) a, c, f, g
 - (b) b, c, f, g
 - (c) b, c, e, f
 - (d) b, d, e, g
9. If an octal-to-binary priority encoder has its 0, 2, 5, and 6 inputs at the active level, the active-HIGH binary output is
 - (a) 110
 - (b) 010
 - (c) 101
 - (d) 000




10. In general, a multiplexer has
- (a) one data input, several data outputs, and selection inputs
 - (b) one data input, one data output, and one selection input
 - (c) several data inputs, several data outputs, and selection inputs
 - (d) several data inputs, one data output, and selection inputs
11. Data distributors are basically the same as
- (a) decoders
 - (b) demultiplexers
 - (c) multiplexers
 - (d) encoders
12. Which of the following codes exhibit even parity?
- (a) 10011000
 - (b) 01111000
 - (c) 11111111
 - (d) 11010101
 - (e) all
 - (f) both answers (b) and (c)

Problems

 1. Find the Boolean expression F implemented by the circuit shown in figure



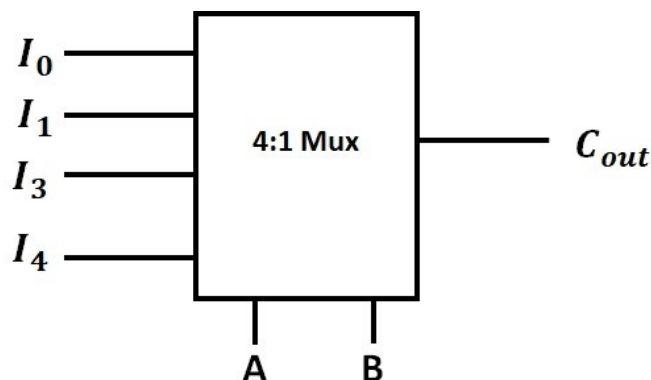
2. A 4:1 multiplexer is to be used for generating the output carry of a full adder. A and B are the bits to be added while C_{in} is the input carry and C_{out} is the output carry. A and B are to be used as the select bits with A being the most significant select bit. What will be the values of the inputs I_0 , I_1 , I_2 , and I_3 so that the output will be C_{out} .






National Institute of Technology Patna

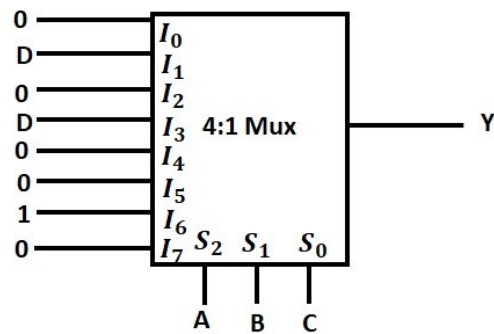
3. What is the output of the following circuit?



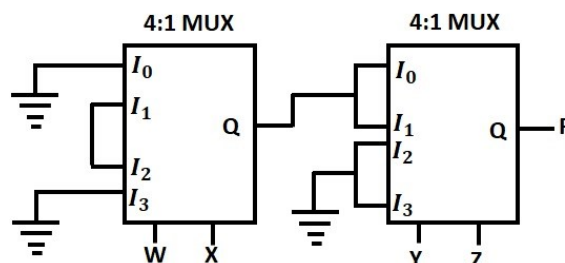
4. Implement a half subtractor by using 2:1 MUX.
5. Determine the output of the following combinational circuit, where W and Y are the MSBs of the control inputs.



 6. Find the Boolean function of F in the given circuit.



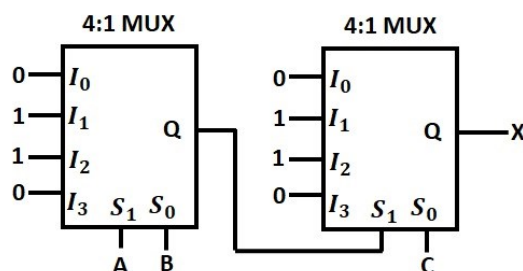7. Derive the logic expressions of Borrow (M) and Difference ($N = X - Y$) for the half subtractor circuit.
8. Design 2-bit magnitude comparator with logic diagram and truth table.
9. What are the limitations of the encoder? Design and explain the 8×4 priority encoder with a valid output.
10. Implement $F(A, B, C, D) = \sum m(2, 3, 5, 7, 8, 9, 12)$ by using 4×1 multiplexer and $\{A, B\}$ as a select line.
11. Implement $P(XOR)Q$ with 4:1 multiplexer.
12. Design 2-input AND gate and 2-input Ex-OR gate by using 2:1 Multiplexer.
13. Determine the logic expression for X in the following circuit



14. Realize 4:1 multiplexer by using 2:1 multiplexer.